
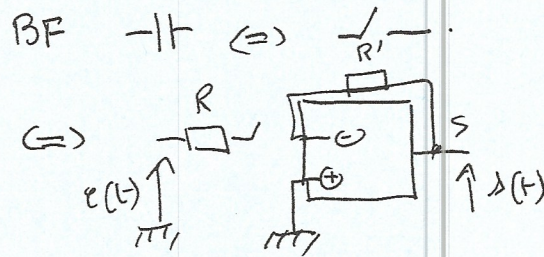


Correction TD Ali


Ex1) Filtrer passe haut du 1^{er} ordre.

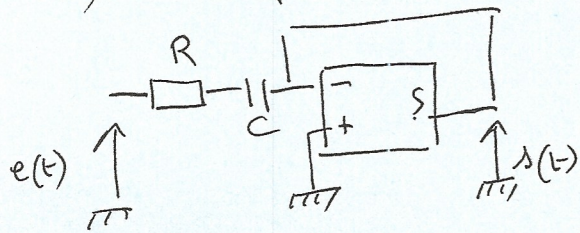

$$V^+ = 0 = V^- \text{ or } V^- = s \Rightarrow s = 0$$

car $i = 0$
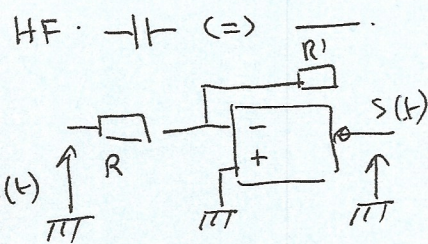
$$V^- = \frac{\frac{e}{R} + \frac{s}{R'}}{\frac{1}{R} + \frac{1}{R'}} = V^+ = 0 \rightarrow \boxed{s = -\frac{R'}{R} e}$$



e) Calcul de H .

$$V^- = \frac{\frac{e}{R + \frac{1}{j\omega C}} + \frac{s}{R'}}{\frac{1}{R + \frac{1}{j\omega C}} + \frac{1}{R'}} = V^+ = 0 \rightarrow$$

$$\frac{s}{e} = \frac{-R'}{R + \frac{1}{j\omega C}} = \frac{-jR'\omega C}{1 + jR\omega C}$$

$$H = \frac{H_{\infty} \cdot j \frac{\omega}{\omega_c}}{1 + j \frac{\omega}{\omega_c}}$$

$$\Rightarrow \begin{cases} \frac{1}{\omega_c} = RC \Rightarrow \omega_c = \frac{1}{RC} \\ \frac{H_{\infty}}{\omega_c} = -R' \Rightarrow \boxed{H_{\infty} = -\frac{R'}{R}} \end{cases}$$

3°] AN $R = 18 \Omega$ et $\omega_c = 10^4 \text{ rad s}^{-1} \rightarrow C = \frac{1}{R\omega_c} = \frac{1}{10^3 \cdot 10^4} = \boxed{10^{-7} \text{ F} = 0,1 \mu\text{F}}$



$$G_{dB}(\infty) = 20 \log |H_{\infty}| = 20 \log \frac{R'}{R} = 20 \text{ dB} \Rightarrow \frac{R'}{R} = 10 \rightarrow \boxed{R' = 108 \Omega}$$

1°) $H \xrightarrow{\text{BF}} H_{\infty} \cdot j \frac{\omega}{\omega_c} \rightarrow G_{dB} \Rightarrow 20 \log |H_{\infty}| + 20 \log x = G_{BF} \quad x = \frac{\omega}{\omega_c}$

$H \xrightarrow{\text{HF}} H_{\infty} \rightarrow G_{dB} \rightarrow 20 \log |H_{\infty}| = 20 \text{ dB}$

$$\varphi \text{ varie de } -\frac{\pi}{2} \text{ à } -\pi$$

$$\varphi = -\frac{\pi}{2} - \arctan x$$

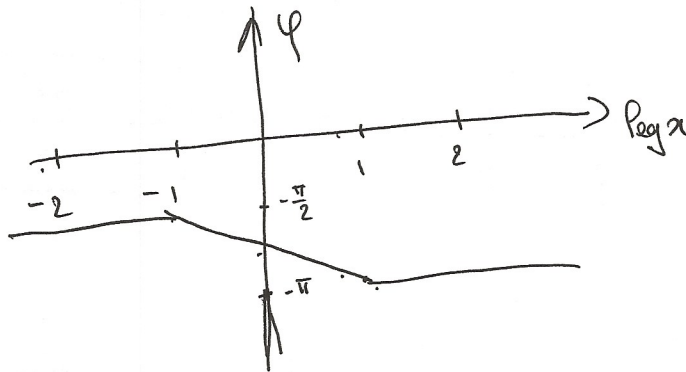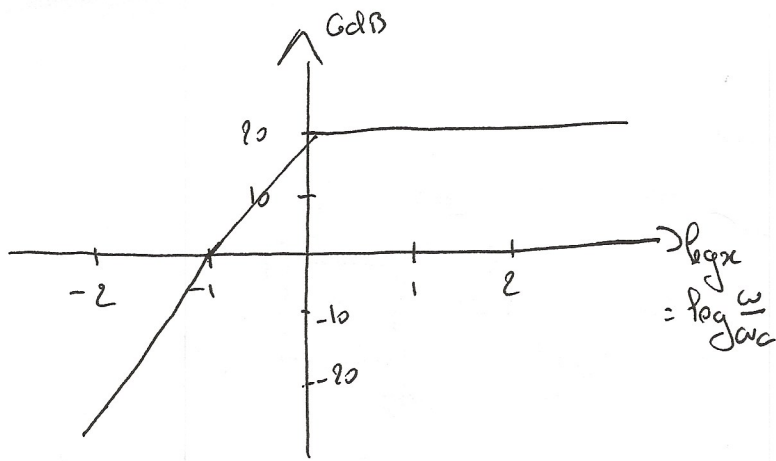

$$\omega_c = 10^4 \text{ rad/s}^{-1}$$

$$\omega_1 = 10^2 \text{ rad/s}^{-1} \rightarrow \alpha_1 = 10^{-2} \rightarrow G_1 = -20 \text{ dB} \quad \varphi_1 = -\frac{\pi}{2}$$

$$\omega_2 = 10^3 \text{ rad/s}^{-1} \rightarrow \alpha_2 = 10^{-1} \rightarrow G_2 = 0 \quad \varphi_2 = -\frac{\pi}{2}$$

$$\omega_3 = 10^5 \text{ rad/s}^{-1} \rightarrow \alpha_3 = 10 \rightarrow G_3 = 20 \text{ dB} \quad \varphi_3 = \frac{\pi}{2}$$



$$G_{dB} = 20 \log |H| \rightarrow |H| = 10^{\frac{G_{dB}}{20}}$$

$$e_1(t) = 1 \cdot \cos \omega_1 t \rightarrow \lambda_1(t) = 0,1 \cos(\omega_1 t - \frac{\pi}{2})$$

$$e_2(t) = 3 \cos \omega_2 t \rightarrow \lambda_2(t) = 3 \cos(\omega_2 t - \frac{\pi}{2})$$

$$e_3(t) = 1 \cos \omega_3 t \rightarrow \lambda_3(t) = 10 \cos(\omega_3 t - \frac{\pi}{2})$$

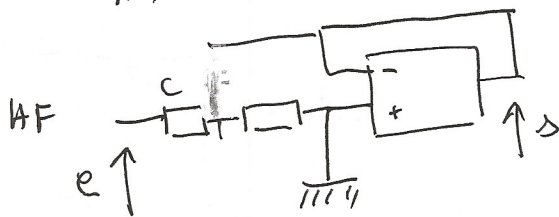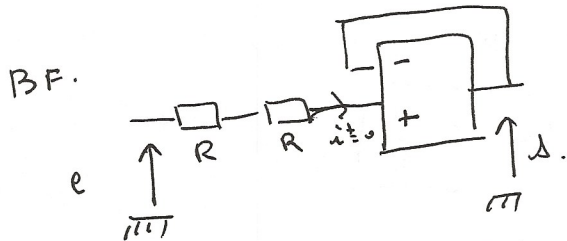ex 2 1] BF -1t ($\Rightarrow$ $\swarrow$)
HF -1t ($\Rightarrow$ $\dashrightarrow$)




$$e - v^+ = 2R \underset{0}{i} = 0 \rightarrow v^+ = e \quad \left. \begin{array}{l} v^+ = v^- = \lambda \\ v^- = \lambda \end{array} \right\} e = \lambda$$

$$\left. \begin{array}{l} v^+ = 0 \\ v^- = \lambda \end{array} \right\} \rightarrow \lambda = 0$$

Filtre passe bas.

2] Calcul de H

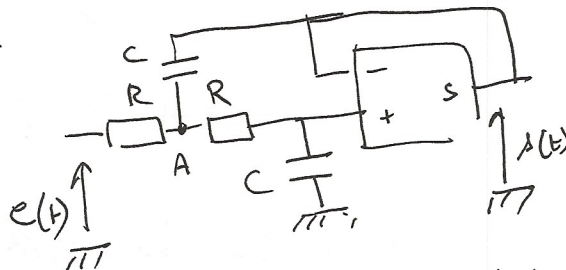

$$v^- = \lambda$$

$$v^+ = \frac{V_A}{\frac{1}{R} + j\omega C} = \frac{V_A}{1 + j\omega RC} = \lambda$$

$$V_A = \frac{\frac{e}{R} + j\omega \lambda + \frac{v^+}{R}}{\frac{1}{R} + j\omega C + \frac{1}{R}} =$$

$$\frac{e + (1 + j\omega RC) \lambda}{2 + j\omega RC} \quad \text{puisque } v^+ = \lambda$$

(2)

En égalant les 2 expressions de V_A :

$$V_A = \frac{e + (1+jR\omega)^{\frac{1}{2}}}{2+jR\omega} = (1+jR\omega)^{\frac{1}{2}} \quad \text{on obtient :}$$

$$\frac{\frac{1}{e}}{\frac{1}{e}} = \frac{1}{1+2jR\omega + (jR\omega)^2} = \frac{H_0}{1+2j\lambda \frac{\omega}{\omega_0} + \left(j\frac{\omega}{\omega_0}\right)^2} \quad \left\{ \begin{array}{l} H_0 = H_{nap} = 1 \\ \omega_0 = \frac{1}{RC} \\ \lambda = 1 > \frac{1}{\sqrt{2}} \text{ pas de } \\ \text{résonance.} \end{array} \right.$$

Calcul de la pulsation de coupure $\alpha_c = \frac{\omega_c}{\omega_0}$.

$$|H|(\alpha_c) = \frac{H_{nap}}{\sqrt{2}} = \frac{1}{\sqrt{2}} \rightarrow (1-\alpha_c^2)^2 + 4\alpha_c^2 = 2$$

$$1 - 2\alpha_c^2 + \alpha_c^4 + 4\alpha_c^2 = 2$$

$$\alpha_c^4 + 2\alpha_c^2 - 1 = 0.$$

$$\Delta = 4 + 4 = 8$$

$$\alpha_c^2 = \frac{-2 + \sqrt{8}}{2} = -1 + \sqrt{2}$$

$$\Rightarrow \alpha_c = \sqrt{\sqrt{2} - 1}$$

$$\Rightarrow \boxed{\omega_c = \sqrt{\sqrt{2} - 1} \cdot \omega_0} \leq 0,6 \omega_0.$$

$$G_{dB}(\alpha_c) = -3 \text{ dB}$$

$$\text{et } G_{dB}(\alpha=1) = 20 \log \frac{1}{\sqrt{2}} = -20 \log 2 = -6 \text{ dB}.$$


$$X_{BF} = 20 \log H_0 = 0.$$

$$X_{HF} = 20 \log H_0 - 40 \log \alpha$$


X_c = signal creneau de fréquence f .

$f_c \rightarrow$ pas de modification.

$f_c \rightarrow$ harmonique 1 "passe"
harmonique 3 atténué

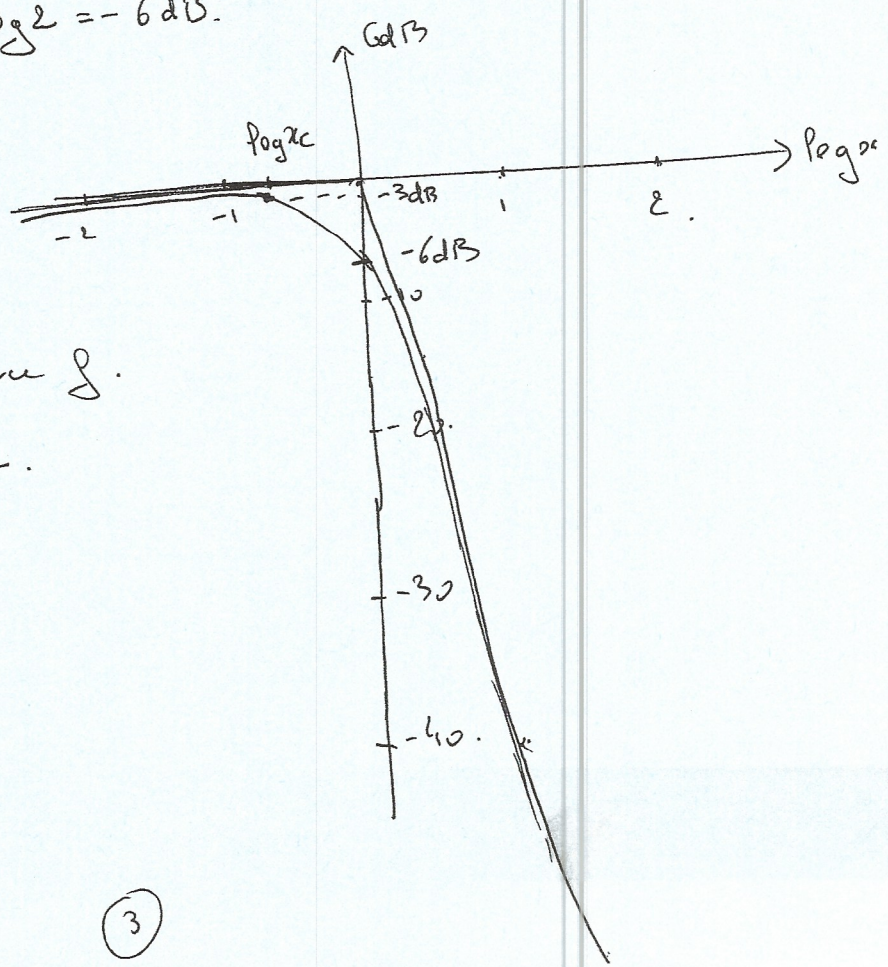

Ex 3

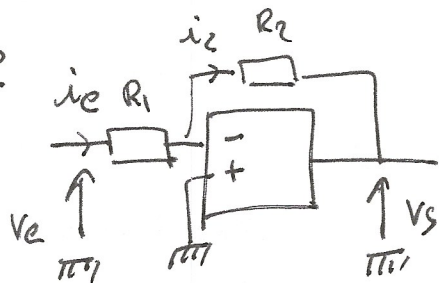

1) l'Al est idéal $\Rightarrow i^+ = i^- = 0$.

$$V^{\ominus} = \frac{V_e}{\frac{1}{R_1} + \frac{1}{R_2}} = 0 \rightarrow \boxed{V_s = -\frac{R_2}{R_1} V_e}$$

$V_e = R_1 i_e$ puisque $V^{\ominus} = 0 \rightarrow Z_e = \frac{V_e}{i_e} = R_1$

2) $V_s = \mu (v^+ - v^-)$ et $\begin{cases} v^+ = 0 \\ V^{\ominus} = \frac{V_e}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_2 \cdot V_e + R_1 \cdot V_s}{R_1 + R_2} \end{cases}$

$$\underline{V_s} = \mu \left(0 - \frac{R_2 V_e + R_1 V_s}{R_1 + R_2} \right) \Rightarrow \underline{V_s} \left[\frac{1}{\mu} + \frac{R_1}{R_1 + R_2} \right] = -\frac{R_2 \cdot V_e}{R_1 + R_2}$$

$$\underline{V_s} \left[\frac{R_1 + R_2}{\mu} + R_1 \right] = -R_2 \cdot V_e$$

$$\underline{V_s} \left[\frac{(R_1 + R_2)(1 + j\frac{\omega}{\omega_c})}{\mu_0} + R_1 \right] = -R_2 \cdot V_e \Rightarrow \underline{V_s} \left[R_1 + R_2 + j(R_1 + R_2)\frac{\omega}{\omega_c} + R_1 \mu_0 \right] = -R_2 \cdot \mu_0 \cdot \underline{V_e}$$

$$\Rightarrow \frac{\underline{V_s}}{\underline{V_e}} = \frac{-R_2 \cdot \mu_0}{R_1 + R_2 + R_1 \mu_0 + j(R_1 + R_2) \cdot \frac{\omega}{\omega_c}}$$

$$= \frac{-\frac{R_2 \mu_0}{R_1 + R_2 + R_1 \mu_0}}{1 + j \left(\frac{R_1 + R_2}{R_1 + R_2 + R_1 \mu_0} \cdot \frac{\omega}{\omega_c} \right)} = \frac{H'_0}{1 + j \frac{\omega}{\omega'_c}}$$

$$\boxed{H'_0 = -\frac{R_2}{R_1 \left[1 + \frac{R_1 + R_2}{R_1 \mu_0} \right]}}$$


$$\omega'_c = \frac{(R_1 \mu_0 + R_1 + R_2) \omega_c}{R_1 + R_2} = \left(1 + \frac{R_1 \mu_0}{R_1 + R_2} \right) \omega_c = \omega'_c$$

$\frac{R_1 + R_2}{R_1} \ll \mu_0 \rightarrow H'_0 \approx -\frac{R_2}{R_1}$

$\omega'_c \rightarrow \frac{R_1 \mu_0}{R_1 + R_2}, \omega_c \gg \omega_c$

4

Q04 Montage de phaseur -

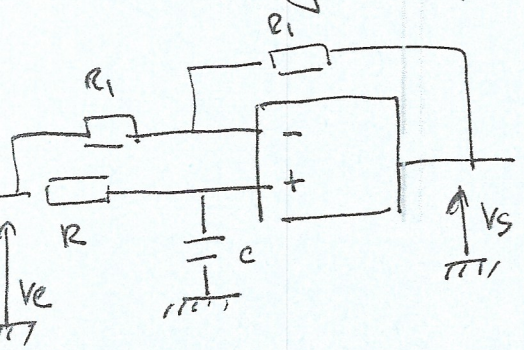

$$V^+ = \frac{V_e}{\frac{1}{R} + j\omega C} = \frac{V_e}{1 + j\omega RC}$$

$$V^- = \frac{\frac{V_e}{R_1} + \frac{V_s}{R_1}}{\frac{2}{R_1}} = \frac{V_e + V_s}{2}$$

$$V^+ = V^- \Rightarrow \frac{V_e}{1 + j\omega RC} = \frac{V_e + V_s}{2} \Rightarrow 2V_e = (1 + j\omega RC)(V_e + V_s)$$


$$V_e (1 - j\omega RC) = (1 + j\omega RC) V_s \Rightarrow$$

$$H = \frac{V_s}{V_e} = \frac{1 - j\omega RC}{1 + j\omega RC}$$

$$|H| e^{j\varphi}$$


$$|H| = 1 \text{ et } \varphi = -2 \arctan \omega RC$$

Montage de phaseur -

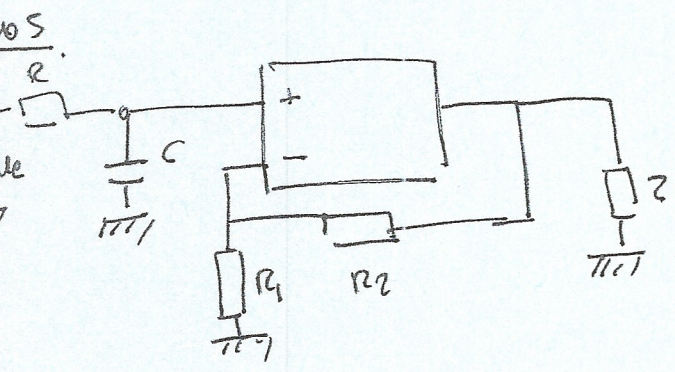

$$BF: \frac{U_s}{U_e} = \frac{R_1 + R_2}{R_1}$$

$$BF: - \Phi \Rightarrow \checkmark$$

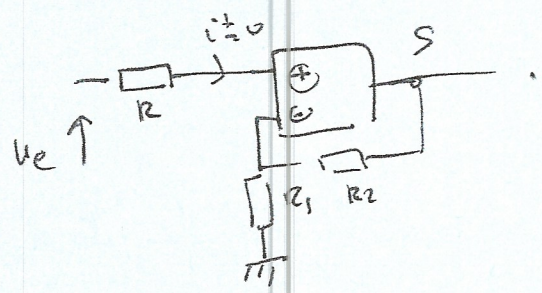

$$V^+ = U_e \text{ (car } i^+ = 0)$$

$$V^- = \frac{\frac{0}{R_1} + \frac{U_s}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1}{R_1 + R_2} U_s$$

$$- \Phi \Rightarrow \Rightarrow V^+ = 0 \text{ donc } V^- \Rightarrow U_s = 0$$

filtre passe bas

Ampl de H:

$$V^+ = \frac{j\omega C \cdot 0 + \frac{U_e}{R}}{\frac{1}{R} + j\omega C} = \frac{U_e}{1 + j\omega RC}$$

$$V^+ = V^- \Rightarrow \frac{U_e}{1 + j\omega RC} = \frac{R_1}{R_1 + R_2} U_s$$

$$\Rightarrow$$

$$\frac{U_s}{U_e} = \frac{\frac{R_1 + R_2}{R_1}}{1 + j\omega RC} = \frac{H_0}{1 + j\frac{\omega}{\omega_c}}$$

$$H_0 = \frac{R_1 + R_2}{R_1} \quad \omega_c = \frac{1}{RC}$$

AN $R = 100 \Omega$
 $C = 10 \mu F = 10^{-5} F$


$$f_c = \frac{\omega_c}{2\pi} = \frac{1}{2\pi} \cdot \frac{1}{RC} = \frac{1}{2\pi} \cdot \frac{1}{10^3} = 159 \text{ Hz}$$

$$H_0 = \frac{R_1 + R_2}{R_1} = \frac{10}{1} = 10$$

dB $\xrightarrow{BF} 20 \log H_0 = 20 \text{ dB} = \gamma_{BF}$
 $\xrightarrow{HF} 20 \log H_0 - 20 \log \omega$

φ varie de 0 à $-\frac{\pi}{2}$.


Exercice 6 Filtrage passe-bande

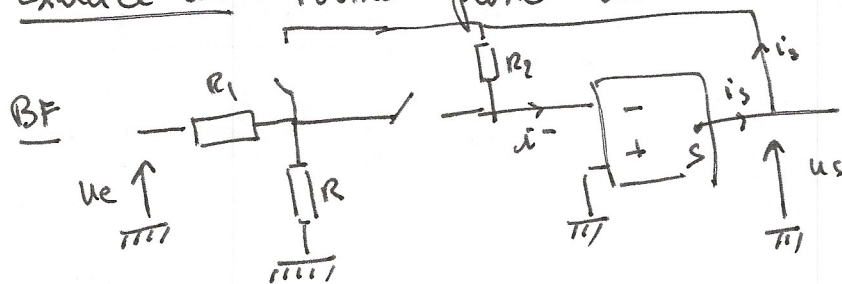

$$V^+ = 0 \Rightarrow V^- = 0$$

$$V^- = u_s = -R_2 i_s = -R_2 i^- = 0$$


$$\Rightarrow u_s = V^- = 0$$

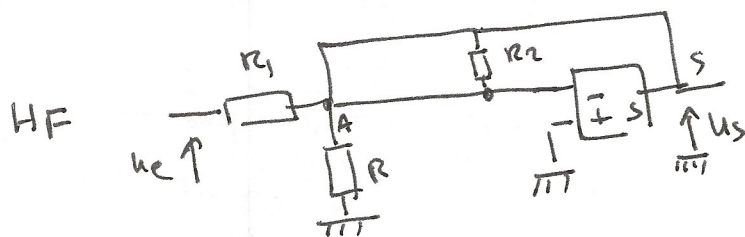

$$V_A = V_S = V^- \rightarrow V_S = 0$$

$$\text{or } V^- = V^+ = 0$$

Filtrage passe-bande

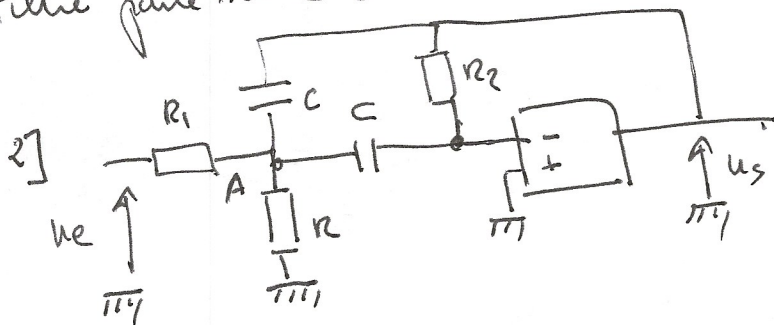

$$V^+ = 0$$

$$V^- = \frac{\frac{u_s}{R_2} + j\omega V_A}{\frac{1}{R_2} + j\omega C} = 0$$

$$\Rightarrow V^- = 0$$

$$V_A = -\frac{u_s}{jR_2 C \omega}$$

$$V_A = \frac{\frac{u_e}{R_1} + \frac{0}{R} + j\omega C u_s}{\frac{1}{R_1} + \frac{1}{R} + j\omega C} = \frac{u_e + j\omega C u_s}{1 + \frac{R_1}{R} + j\omega R_1 C} = \frac{R u_e + j\omega R R_1 C u_s}{R + R_1 + j\omega R R_1 C} = -\frac{u_s}{j\omega R_2 C}$$

$$[R u_e + j\omega R R_1 C u_s] j\omega R_2 C = -[R + R_1 + j\omega R R_1 C] u_s$$

$$\frac{u_s}{u_e} = \frac{-j\omega R R_2 C}{R + R_1 + j\omega R R_1 C + R R_1 R_2 C^2 (j\omega)^2} = \frac{-j\omega R R_2 C}{1 + j\frac{R R_1}{R + R_1} \omega C + \frac{R R_1 R_2 C^2}{R + R_1} \omega^2}$$

A identifieri $\hat{a}$. $\underline{H} = \frac{H_0 \cdot j\omega}{Q\omega_0}$

$$1 + j\frac{\omega}{Q\omega_0} + \left(j\frac{\omega}{\omega_0}\right)^2$$

$$d'au \begin{cases} \frac{1}{\omega_0^2} = \frac{R R_1 R_2}{R + R_1} \cdot C^2 \\ \frac{1}{Q\omega_0} = \frac{R R_1 C}{R + R_1} \\ \frac{H_0}{Q\omega_0} = \frac{-R R_2 C}{R + R_1} \end{cases}$$

$$\rightarrow \left| \omega_0 = \sqrt{\frac{R + R_1}{R R_1 R_2}} \cdot \frac{1}{C} \right|$$

$$\rightarrow \left| H_0 = -\frac{R_2}{R_1} \right|$$

$$d' \left| Q = \sqrt{\frac{R_2 (R + R_1)}{R R_1}} \right|$$

q) $H_0 = -2$ $Q = 10$


$\underline{H} \xrightarrow{BF} \frac{H_0 \cdot j\omega}{Q} \Rightarrow \gamma_{BF} = 20 \log \frac{|H_0|}{Q} + 20 \log \omega$ et $\varphi_{BF} = -\pi + \frac{\pi}{2} = -$

$\underline{H} \xrightarrow{HF} \frac{H_0 \cdot j\omega}{Q (j\omega)^2} = \frac{H_0}{Q} \cdot \frac{1}{j\omega} \rightarrow \gamma_{HF} = 20 \log \frac{|H_0|}{Q} - 20 \log \omega$ et $\varphi_{HF} = -$

I | $\omega = 1$.
 $20 \log \frac{|H_0|}{Q}$

AN $20 \log \frac{|H_0|}{Q} = 20 \log \frac{2}{10} = 20 \log 2 - 20 \log 10$
 $= 6 - 20 = -14 \text{ dB}$


$\begin{cases} G_{max} = 20 \log |H_0| = 20 \log 2 = 6 \text{ dB} \\ \varphi(\omega=1) = -\pi \end{cases}$

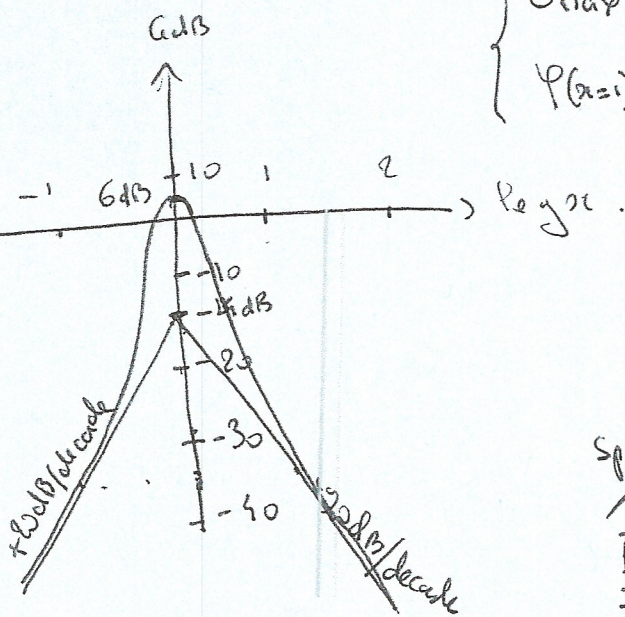


$$u_e(t) = 5 + 3 \cos(2\pi 80 t) - 2 \sin(2\pi (380) t)$$

$$u_s(t) = 0 + 6 \cos(2\pi (80) t + \pi) - \underbrace{2 \cdot 1}_{0,15} \underbrace{H(\omega=3) \sin(2\pi (380) t)}_{+\varphi(\omega=3) + \frac{\pi}{2}}$$


Spectre de $u_e(t)$

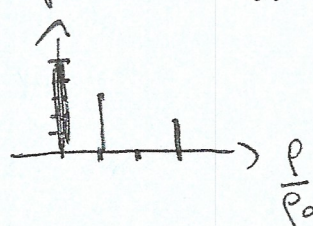

spectre de $u_s(t)$

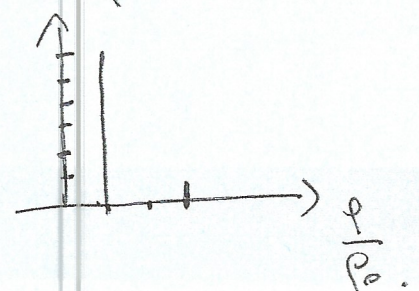

Ex 7 Filtrage réactif.

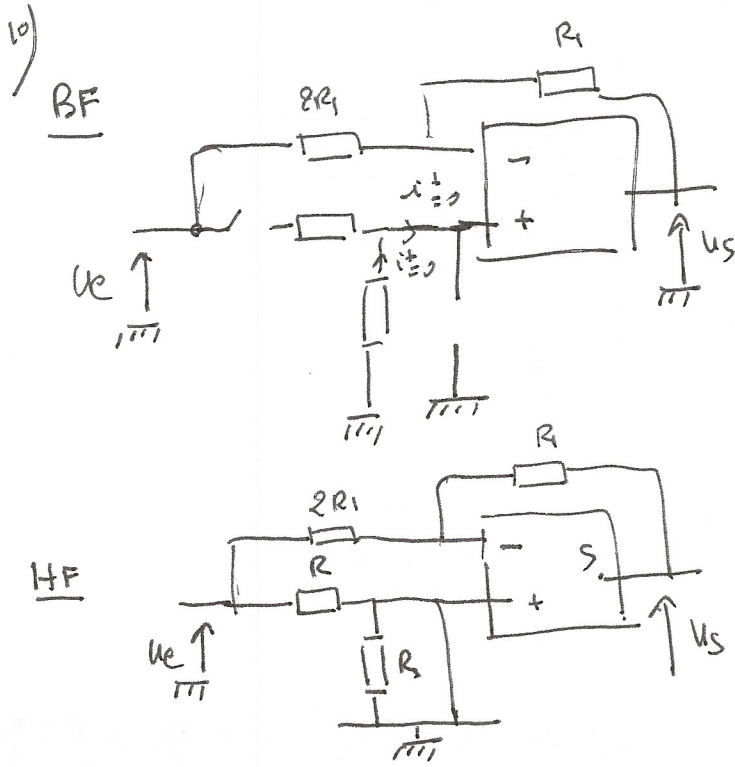

$$V^+ = 0$$


$$V^- = \frac{\frac{U_e}{2R_1} + \frac{U_s}{R_1}}{\frac{1}{2R_1} + \frac{1}{R_1}}$$

$$V^+ = V^- \Rightarrow \boxed{U_s = -\frac{U_e}{2}}$$

$V^+ = 0$ et V^- a tjs la même expression

$$\boxed{U_s = -\frac{U_e}{2}}$$

11) Calcul de la fonction de transfert:

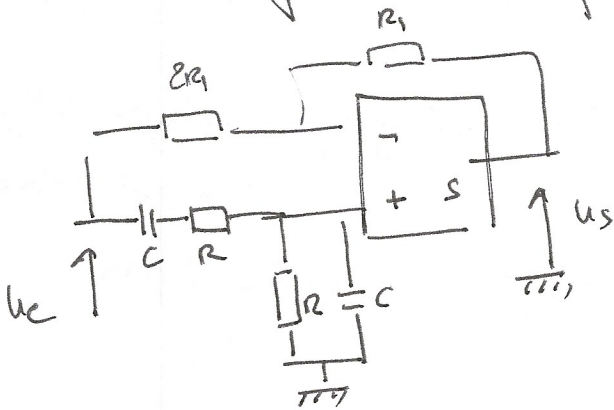

$$V^- = \frac{\frac{U_e}{2R_1} + \frac{U_s}{R_1}}{\frac{1}{2R_1} + \frac{1}{R_1}} = \frac{U_e + U_s}{3}$$

$$V^+ = \frac{\frac{U_e}{R + \frac{1}{j\omega C}} + \frac{0}{Z_{eq}}}{\frac{1}{R + \frac{1}{j\omega C}} + \frac{1}{Z_{eq}}}$$

$$\begin{aligned} V^+ &= \frac{j\omega C U_e}{1 + j\omega RC} \\ &= \frac{j\omega C}{1 + j\omega RC} + \frac{1}{R} j\omega C \\ &= \frac{U_e + 2U_s}{3} \end{aligned}$$

Après calculs

$$\frac{U_s}{U_e} = -\frac{1}{2} \frac{(1 + (j\omega RC)^2)}{1 + 3j\omega RC + (j\omega RC)^2}$$

$$H_0 \frac{(1 - \alpha^2)}{1 - \alpha^2 + j\frac{\omega}{Q}}$$

$$\begin{cases} H_0 = -\frac{1}{2} \\ \frac{1}{\omega_0} = RC \rightarrow \omega_0 = \frac{1}{RC} \\ \frac{1}{Q} = 3RC \rightarrow Q = \frac{1}{3} \end{cases}$$

2

$$\underline{H} = \frac{H_0}{1 + \frac{j\omega/\varphi}{1-\alpha^2}} = \frac{H_0}{1 + \frac{1}{\varphi\left(\frac{1}{\alpha} - \alpha\right)}} = \frac{H_0}{1 + \frac{1}{j\varphi\left(\alpha - \frac{1}{\alpha}\right)}}$$

$$\alpha \rightarrow 0 \quad \underline{H} \rightarrow H_0$$


$$\gamma_{BF} = 20 \log H_0$$

$$\alpha \rightarrow \infty \quad \underline{H} \rightarrow H_0$$

$$\gamma_{HF} = 20 \log H_0$$

$$\alpha = 1 \quad \underline{H} \rightarrow 0$$

$$G_{dB} \rightarrow -\infty$$

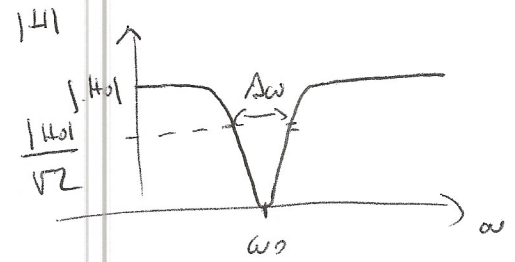

$$|\underline{H}(\omega)| = |\underline{H}(\omega_0)| = \frac{|H_{notch}|}{\sqrt{2}} = \frac{H_0}{\sqrt{2}} \rightarrow Q = 1 + \frac{1}{\varphi^2\left(\alpha - \frac{1}{\alpha}\right)^2}$$

$$\Rightarrow \left(\alpha - \frac{1}{\alpha}\right) = \pm \frac{1}{\varphi} \quad \Rightarrow \quad \frac{\omega_0}{\Delta\omega} = Q$$